

CASE WESTERN RESERVE UNIVERSITY
ECES 318
HW 4
Fall 2015

Due Nov 12, 2015

NAME:

| Problem | Scale | Score |
|---------|-------|-------|
| 1 | 50 | |
| 2 | 50 | |
| 3 | 50 | |
| 4 | 50 | |
| total | 200 | |

Problem 1. [50 points]

You are asked to design and write a VHDL model and verify its correctness for a circuit that is capable of adding and subtracting signed and unsigned numbers based on a 3-bit input code, carry output enable bit, and input carry bit. The code input will command the adder to perform one of six functions on the two 16-bit word inputs. The adder will output the result of the 16-bit function, a signed overflow bit, and a carry out bit if the carry output enable input bit is set. This circuit will be asynchronous, so it will not contain any memory elements to operate. The details about the input/output signals and control functions are outlined below.


```

TOP MODULE: Adder
PRIMARY SIGNALS: BUS inputs/outputs and additional signals
  BUS signals: bit 15 is the most significant bit. All
  bus signals are named with upper case letters.
  INPUTS:
    A[15:0]
    B[15:0]
    CODE[2:0]
  OUTPUTS:
    C[15:0]

  Additional signals: named with lower case letters
    vout = signed overflow
    cout = carry output
    cin  = carry input
    coe  = carry output enable (active low)

  3-bit CODE[2:0] control signals
    add  : 000      signed addition      (A+B -> C)
    addu : 001      unsigned addition    (A+B -> C)
    sub  : 010      signed subtraction   (A-B -> C)
    subu : 011      unsigned subtraction (A-B -> C)
    inc  : 100      signed increment      (A+1 -> C)
    dec  : 101      signed decrement      (A-1 -> C)

```

 

Here are the input/output:

```

A = A(15:0);      B = B(15:0)
i = cin           oe = coe
f = function      C = C(15:0)
v = vout          cout = cout

```

| A | B | i | oe | f | C | v | cout |
|------|------|---|----|------|------|---|------|
| 0000 | 0001 | 0 | 0 | add | 0001 | 0 | 0 |
| 000F | 000F | 1 | 0 | add | 001F | 0 | 0 |
| 7F00 | 0300 | 0 | 0 | add | 8200 | 1 | 0 |
| FF00 | 0100 | 1 | 0 | add | 0001 | 0 | 1 |
| 8100 | 8000 | 1 | 1 | add | 0101 | 1 | d |
| | | | | | | | |
| 0000 | 0001 | 0 | 0 | addu | 0001 | 0 | 0 |
| 000F | 000F | 1 | 0 | addu | 001F | 0 | 0 |
| 7F00 | 0300 | 0 | 0 | addu | 8200 | 0 | 0 |
| FF00 | 0100 | 1 | 0 | addu | 0001 | 0 | 1 |
| 8100 | 8000 | 1 | 1 | addu | 0101 | 0 | d |
| | | | | | | | |
| 0000 | 0001 | 1 | 0 | sub | FFFF | 0 | 0 |
| 000F | 000F | 1 | 0 | sub | 0000 | 0 | 1 |
| 7F00 | 0300 | 1 | 0 | sub | 7C00 | 0 | 1 |
| FF00 | 0100 | 1 | 0 | sub | FE00 | 0 | 1 |
| 8100 | 8000 | 1 | 1 | sub | 0100 | 0 | d |
| | | | | | | | |
| 0000 | 0001 | 1 | 0 | subu | FFFF | 0 | 0 |
| FF00 | FCE0 | 1 | 0 | subu | 0220 | 0 | 1 |
| 7F00 | 0300 | 1 | 0 | subu | 7C00 | 0 | 1 |
| FF00 | 0100 | 1 | 0 | subu | FE00 | 0 | 1 |
| 8100 | 8000 | 1 | 1 | subu | 0100 | 0 | d |
| | | | | | | | |
| 0000 | 0100 | 0 | 0 | inc | 0001 | 0 | 0 |
| 0F00 | 0F00 | 1 | 0 | inc | 0F01 | 0 | 0 |
| 7FFF | 0300 | 0 | 0 | inc | 8000 | 1 | 0 |
| FF00 | 0100 | 1 | 0 | inc | FF01 | 0 | 0 |
| 8100 | 8000 | 1 | 1 | inc | 8101 | 0 | d |
| | | | | | | | |
| 0000 | 0100 | 0 | 0 | dec | FFFF | 0 | 0 |
| 000F | 000F | 1 | 0 | dec | 000E | 0 | 1 |
| 7F00 | 0300 | 0 | 0 | dec | 7EFF | 0 | 1 |
| FF00 | 0100 | 1 | 0 | dec | FEFF | 0 | 1 |
| 8000 | 8000 | 1 | 1 | dec | 7FFF | 1 | d |

d = don't care

Signed overflow: When two operands of the same sign are added together and the result is of the opposite sign. Be sure that the signed overflow bit vout is only affected by signed operations.

Here is an example of signed overflow. You must determine all the cases when signed overflow will occur.


```

Ex:          01110000      8 bit signed int
            +01000001      8 bit signed int
            -----
            10110001      vout=1

```

Problem 2. [50 points]

Analyze the logic circuit given below.

 

- Write a structural VHDL Model for this design and simulate your circuit to verify correctness. (Explain your approach)
- Write a behavioral VHDL model and verify that your model is equivalent to the given circuit.

Problem 3. [50 points]

Multiplication of signed operands, which generate a double-length product in the 2's-complement number system. The general strategy is the accumulate partial products by adding versions of the multiplicand as selected by the multiplier bits.

First, consider the case of a positive multiplier and a negative multiplicand. When we add a negative multiplicand to a partial product, we must extend the sign-bit value of the multiplicand to the left as far as the product will extend (as shown in the figure below). The sign extension of the multiplicand is hand-written.

| | | | | | | | | | | |
|---|--|--|--|--|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|--|
| | | | | | 1 0 | 0 1 | 0 0 | 1 1 | 1 1 | MULTIPLICAND (-13) MULTIPLIER (+11) |
| | 1 1 0 1 0 | 1 1 0 1 0 | 1 1 0 0 0 | 1 1 0 0 0 | 1 0 0 1 0 | 0 0 0 1 0 | 0 1 0 1 0 | 1 1 0 1 0 | 1 1 0 1 0 | |
| 1 | 1 | 0 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | PRODUCT |

For a negative multiplier, a straightforward solution is to form the 2's complement of both multiplier and multiplicand and proceed as in the first case.

- Write a VHDL file to model the above behavior for 5 bits multiplier and 5 bits multiplier.
- Use Modelsim to compile your VHDL file.
- Use Modelsim to simulate your multiplier with the following cases: $(-11*4, 14*-3, -11*-12)$

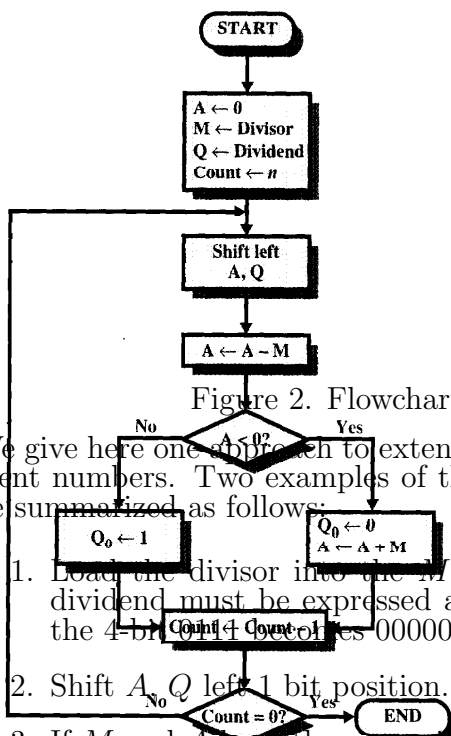


Figure 2. Flowchart of division of unsigned binary integers.

We give here one approach to extend the division algorithm to handle negative two's complement numbers. Two examples of this approach are shown in Figure 3. The algorithm can be summarized as follows:

1. Load the divisor into the M register and the dividend into the A, Q registers. The dividend must be expressed as a $2n$ -bit two's complement number. Thus for example, the 4-bit numbers 00001111 and 1001 becomes 11111001 .
2. Shift A, Q left 1 bit position.
3. If M and A have the same signs, perform $A = A - M$; otherwise, $A = A + M$.
4. The preceding operation is successful if the sign of A is the same before and after the operation.
 - a. If the operation is successful or $A = 0$, then set $Q_0 = 1$.
 - b. If the operation is unsuccessful and $A \neq 0$, then set $Q_0 = 0$ and restore the previous value of A .
5. Repeat steps 2 through 4 as many times as there are bit positions in Q .
6. The remainder is in A . If the signs of the divisor and dividend were the same, then the quotient is in Q ; otherwise, the correct quotient is the two's complement of Q .

Figure 3. Example of twos complement division.

- a) Write a VHDL file to model the above behavior for 4 bits Divisor and 4 bits dividend.
 b) Use Modelsim to compile your VHDL file.
 c) Use Modelsim to simulate your division circuit with the following cases: $7/-2$, $6/-2$.

| A | Q | M = 0011 | A | Q | M = 1101 |
|----------------|------|---------------|-----------------|------|---------------|
| 1111 | 1001 | Initial value | 1111 | 1001 | Initial value |
| 1111 | 0010 | shift | 1111 | 0010 | shift |
| 0010 | | add | 0010 | | subtract |
| 1111 | 0010 | restore | 1111 | 0010 | restore |
| 1110 | 0100 | shift | 1110 | 0100 | shift |
| 0001 | | add | 0001 | | subtract |
| 1110 | 0100 | restore | 1110 | 0100 | restore |
| 1100 | 1000 | shift | 1100 | 1000 | shift |
| 1111 | | add | 1111 | | subtract |
| 1111 | 1001 | set $Q_0 = 1$ | 1111 | 1001 | set $Q_0 = 1$ |
| 1111 | 0010 | shift | 1111 | 0010 | shift |
| 0010 | | add | 0010 | | subtract |
| 1111 | 0010 | restore | 1111 | 0010 | restore |
| (c) $(-7)/(3)$ | | | (d) $(-7)/(-3)$ | | |