

# Logic Simulation

- Purpose
  - ◆ **Design Verification**
  - ◆ **Performance Evaluation**
  - ◆ **Evaluation of Alternative Designs**
  - ◆ **Debugging**
    - ▲ observe internal signals
    - ▲ can change clock rate, gate delays
    - ▲ can start the simulation in any desired state
    - ▲ can be interfaced to partial designs

# Outline

- Types of Simulation
- Logic Simulation in Presence of Unknowns
- Simulation of Synchronous Sequential Circuits
- Gate Evaluation Methods
- Event-Driven Simulation
- Hazard Detection

## Types of Simulation


- Compiled Code
  - ◆ functional verification, timing not incorporated
- Table Driven
  - ◆ primitives are evaluated using tables
- Event Driven (activity-directed)
  - ◆ 1% - 10% of lines are active in a simulation
- Time Driven / Cycle Based

**Event:** change in signal line --> “active line”  
Evaluate gates only when inputs change.  
Level of simulation depends on level of the model.

## Unknown Value


- Unlike real circuits, which have only two signal values (0, 1), a simulator cannot restrict itself to 0, 1. Why? (0, 1, U, Z, Rising, Falling)
- At the start, flip-flops are in an “unknown” state.
- Formally, unknown is a set of two values {0,1}
  - ◆ Boolean Operation  $op$
  - ◆  $0 \text{ op } U = \{0\} \text{ op } \{0,1\} = \{0 \text{ op } 0, 0 \text{ op } 1\}$
  - ◆  $op = \text{AND}$ 
    - ▲  $0 \text{ AND } U = \{0 \text{ AND } 0, 0 \text{ AND } 1\} = \{0,0\} = \{0\} = 0$
    - ▲  $1 \text{ AND } U = \{1 \text{ AND } 0, 1 \text{ AND } 1\} = \{0,1\} = U$

## Unknown Value

 

- A subtle difference between unknown U and don't care X
- In Boolean algebraic operations, they are the same, but when differences do exist, care must be taken.
 
## Logic Simulation in Presence of Unknowns



- Use high-level Boolean functions of modules.

## Coding for Three Values

- Values: 0, 1, U
- An encoding: 00, 11, 01

AND

	0	1	x
0	0	0	0
1	0	1	x
x	0	x	x

AND

	00	11	01
00	00	00	00
11	00	11	01
01	00	01	01

bit-wise AND  
on the codes

0: 00  
AND  $\frac{1: 11}{0: 00}$


U: 01  
AND  $\frac{1: 11}{U: 01}$

0: 00  
OR  $\frac{1: 11}{1: 11}$

U: 01  
OR  $\frac{1: 11}{1: 11}$

NOT 00  $\rightarrow \bar{0}\bar{0} \rightarrow 11$   
NOT U  $\rightarrow \bar{0}\bar{1} \rightarrow 10 \xrightarrow{\text{swap}} 01$
 
## Simulation of Synchronous Sequential Circuits



Procedure CKT1  
inputs A, B; static Q;  
begin  
    E = B NAND Q  
    F = A OR B  
    Q = F  
end

Every call advances  
the clock by 1.

Assume data is stable at inputs to  
flip-flops when clock signal arrives

# Gate Evaluation Methods


**Controlling** value and **Inversion** value:

- Controlling value controls the output of the gate
- If there is a controlling input, output of gate is  $c \oplus i$   
otherwise  $c' \oplus i$


	c	i
AND	0	0
OR	1	0
NAND	0	1
NOR	1	1
 
# Gate Evaluation Methods

- Input scanning
  - ♦ Look for controlling value c
  - ♦ If found then output = c
  - ♦ else if unknown found then output = X
  - ♦ else output = c
- Count based
  - ♦  $C_0$  = count of 0's
  - ♦  $C_x$  = count of x's
  - ♦ if  $C_0 > 0$  then output 0
  - ♦ else if  $C_x > 0$  then output x
  - ♦ else output 1
- Table based -- indexed look-up



## Table-Based Indexed Look-up

 

- $\{0, 1, x\}^3 = 27$  possible vectors
- $2^6 = 64$  entries in table, since 0,1,x require 2 bits

Index I = 

--	--	--	--


 0

A	B	C	D[I]
00	00	00	0
00	00	01	0
	...		
11	11	11	1

Of 64 entries, 27 are useful

**zoom tables:** gate type is part of index

## Event-Driven Simulation

 




- All  $\tau = 0$ : zero delay simulation
  - ♦ **easiest, fastest**
- All  $\tau = 1$ : unit delay simulation
  - ♦ **moderate**
- Different  $\tau$ 's: variable delay, assignable delay simulation
  - ♦ **hardest, slowest**

# Event-Driven Simulation

- Different gates may have different delays
  - ♦ In the project you will implement a zero-delay simulator
- **Logic Simulation Algorithm with Delay**
  - Two-pass strategy when delay is not zero:
    - ♦ Need to schedule events, that is, changes of logic values
    - ♦ Need to keep a queue of activated gates
   
## Observation on Logic Simulation Algorithm with Delay


- Correct only if an event at time  $t+k$  does not schedule an event earlier than an already scheduled event for the same gate.
- Example:



### event list


- 0: (a,0)
  - 1: (a,1)
  - 6: (e,0)
  - 2: (d,0)
  - 4: (e,1)
- Need to cancel 6: (e,0)

## Zero-Delay vs. Unit-Delay Simulation

 


- In unit-delay simulation, gate A is evaluated 3 times
- In zero-delay simulation, gate A is evaluated once
  - ♦ zero-delay gives steady-state values of nodes

## Zero-Delay Simulation Example

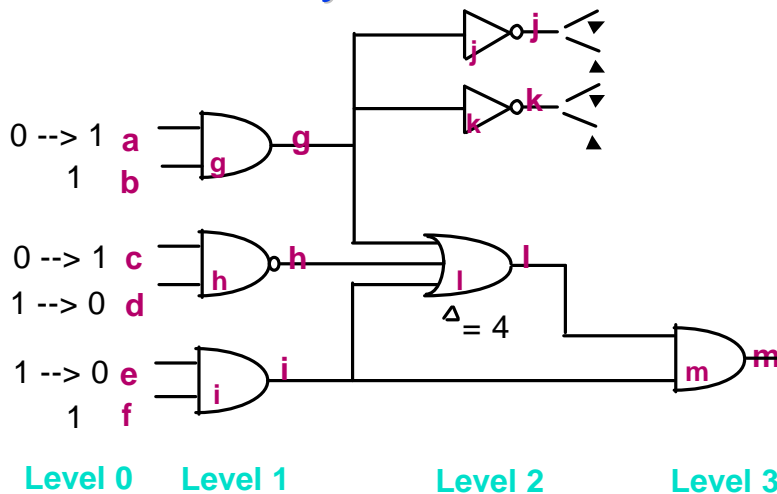



## Assigned-Delay Simulation Example

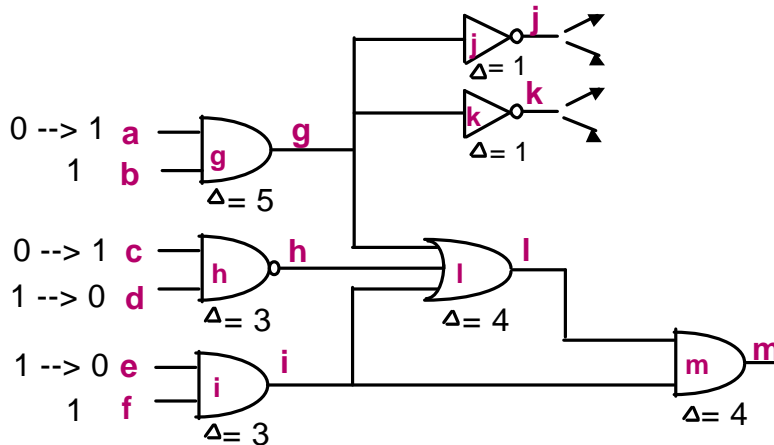

## Assigned-Delay Simulation Example

### Time $t_1$

Pass 1:  $a \neq a' \rightarrow (a'1)$  is an event, add **g** to Activated  
 $c \neq c' \rightarrow (c'1)$  is an event, add **h** to Activated  
 $d \neq d' \rightarrow (d'0)$  is an event, add **h** to Activated  
 $e \neq e' \rightarrow (e'1)$  is an event, add **i** to Activated

Pass 2:  $g' = 1$  at time  $1+5 = 6$   
 $h' = 1$  at time  $1+3 = 4$   
 $i' = 0$  at time  $1+3 = 4$

### Time $t_4$

Pass 1:  $h' = h$ , so no event  
 $i' \neq i \rightarrow (i',0)$  is an event, add **l**, **m** to Activated

Pass 2:  $l' = 1$  at time  $4+4 = 8$   
 $m' = 0$  at time  $4+4 = 8$

## Assigned-Delay Simulation Example

### Event List

t1: (a',1), (c',1), (d',0), (e',0)

t6: (g',1)

t4: (h',1), (i',0) ← Must schedule since there may be  
 t8: (l',1), (m',0) (h,0) scheduled before time t4


t7: (j',0), (k',0)

t10: (l',1)


Time Event

t6: (g',1) means at time t6, g will take on value 1.

## Unit-Delay Simulation Example

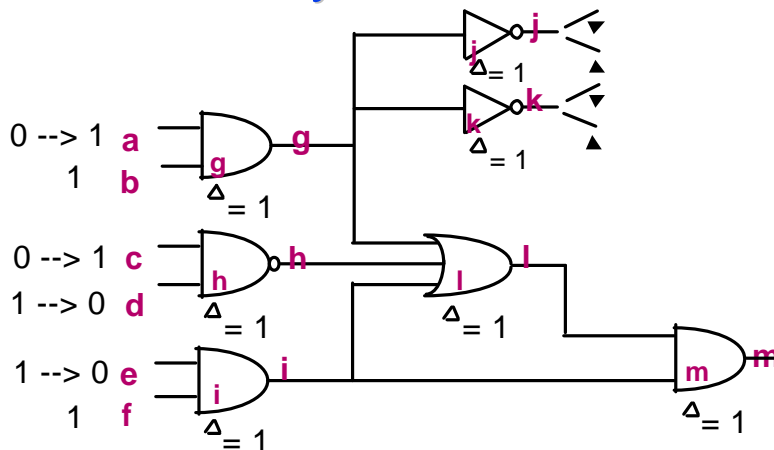

# Hazard Detection

 

- Important for unclocked flip-flops (latches)
  - ◆  $t$ :  $A=0, B=1 \rightarrow 1$
  - ◆  $t'$ :  $A=U, B=U \rightarrow U$   $\underline{1 \ U \ 1}$
  - ◆  $t+1$ :  $A=1, B=0 \rightarrow 1$
- Hazard exists if and only if the output sequence has 0U0 or 1U1